

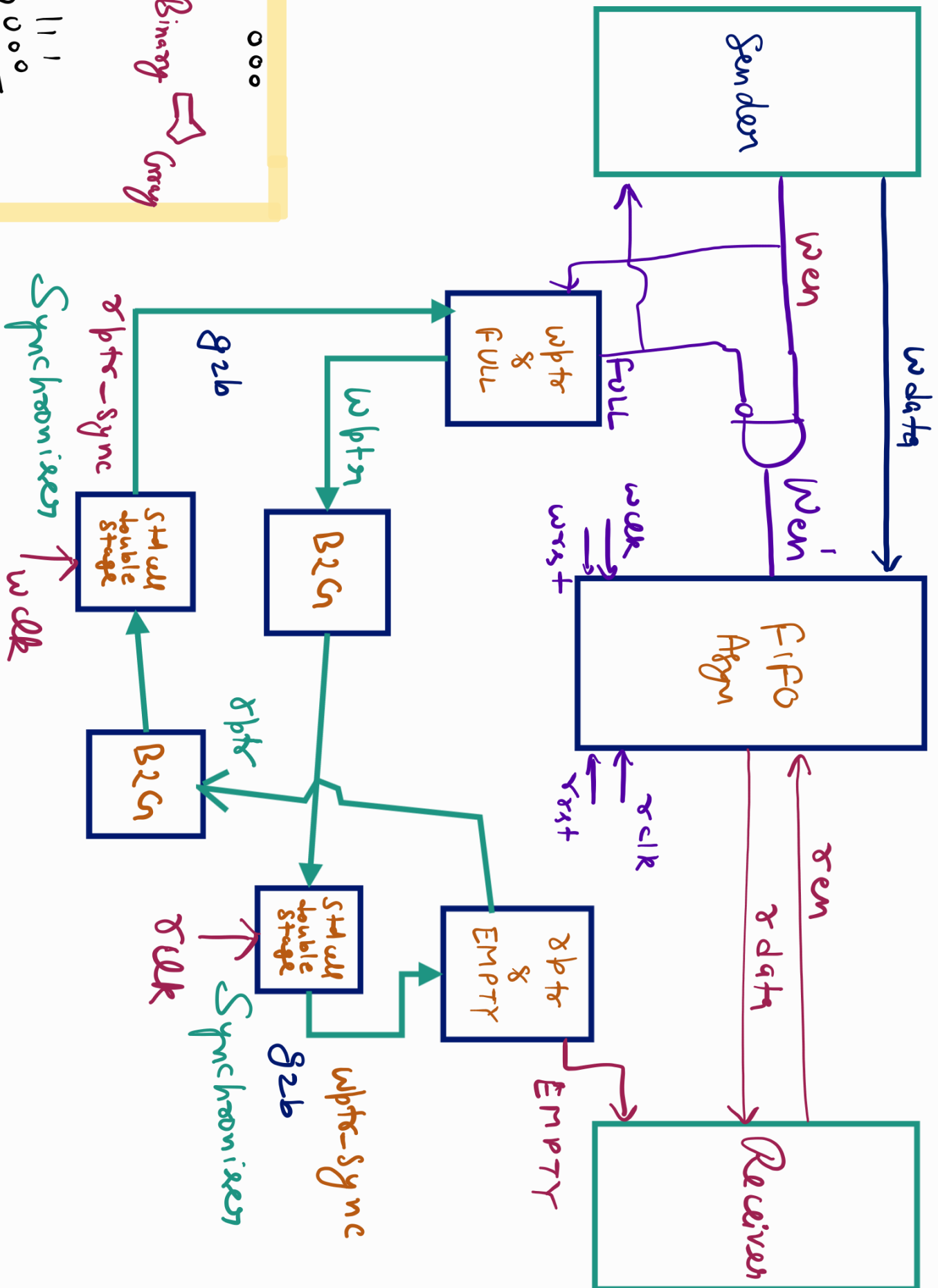


Asynchronous FIFO

 

Limitation of A. FIFO

6 deep FIFO

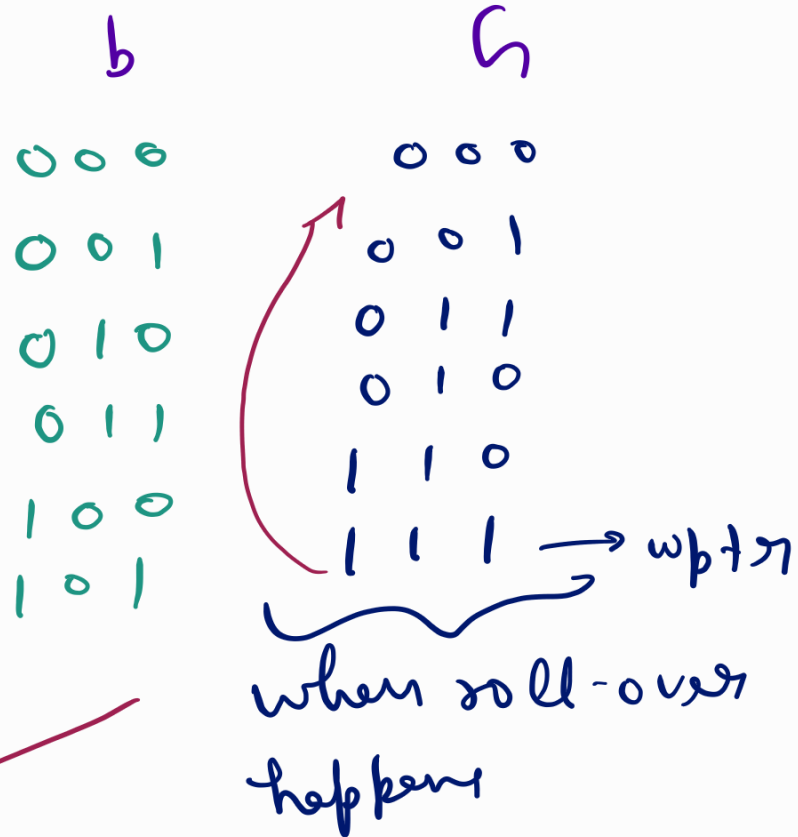


111 → 000

All bits toggled


→ Again lead to
Meta-stability State

Asynchronous FIFO

In asynchronous FIFO, data read and write operations use different clock frequencies. Since write and read clocks are not synchronized, it is referred to as asynchronous FIFO. Usually, these are used in systems where data need to pass from one **clock domain** to another which is generally termed as '**clock domain crossing**'. Thus, **asynchronous FIFO helps to synchronize data flow** between two systems working on different clocks.

 

Asynchronous FIFO Block Diagram

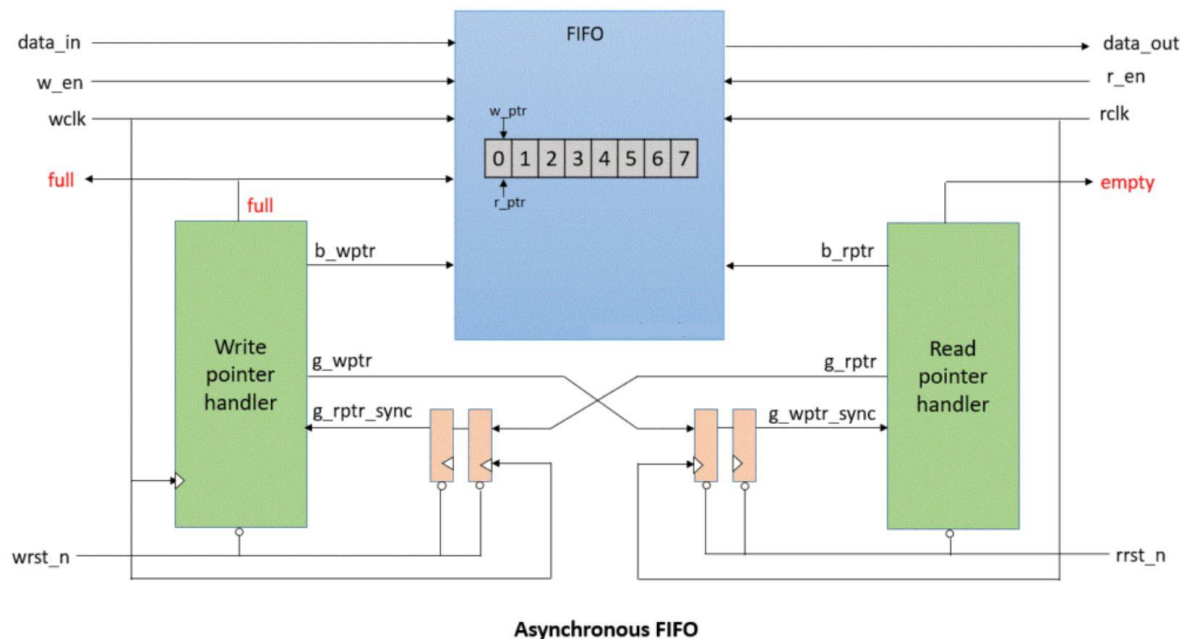

SYNCHRONIZERS will help to achieve clock domain crossing.

A single "2 FF synchronizer" can resolve metastability for only one bit. Hence, depending on write and read pointers multiple 2FF synchronizers are required.

Signals:

wr_en: write enable

wr_data: write data

full: FIFO is full

empty: FIFO is empty

rd_en: read enable

rd_data: read data

b_wptr: binary write pointer

g_wptr: gray write pointer

b_wptr_next: binary write pointer next

g_wptr_next: gray write pointer next

b_rptr: binary read pointer

g_rptr: gray read pointer

b_rptr_next: binary read pointer next

g_rptr_next: gray read pointer next

b_rptr_sync: binary read pointer synchronized


b_wptr_sync: binary write pointer synchronized

old

Asynchronous FIFO Operation

In the case of synchronous FIFO, the write and read pointers are generated on the same clock. However, in the case of asynchronous FIFO write pointer is aligned to the write clock domain whereas the read pointer is aligned to the read clock domain. Hence, it requires domain crossing to calculate FIFO full and empty conditions. This causes metastability in the actual design. In order to resolve this metastability, 2 flip flops or 3 flip flops synchronizer can be used to pass write and read pointers. For explanation, we will go with 2 flip-flop synchronizers. Please note that a single "2 FF synchronizer" can resolve metastability for only one bit. Hence, depending on write and read pointers multiple 2FF synchronizers are required.

 The write operation occurs in one clock domain, and the read operation occurs in another clock domain.



2 flip-flop synchronizer

```

module synchronizer #(parameter WIDTH=3) (input clk, rst_n, [WIDTH:0] d_in,
output reg [WIDTH:0] d_out);
  reg [WIDTH:0] q1;
  always@(posedge clk) begin
    if(!rst_n) begin
      q1 <= 0;
      d_out <= 0;
    end
    else begin
      q1 <= d_in;
      d_out <= q1;
    end
  end
end
endmodule

```

Handwritten annotations: "Internal Register" (pink oval around the first flip-flop and its inputs) and "Always Block" (pink oval around the always block in the code).

Usage of Binary to Gray code converter and vice-versa in Asynchronous FIFO

Till now, we discussed how to get asynchronous write and read pointers in respective clock domains. However, we should not pass binary formatted write and read pointer values. Due to metastability, the overall write or read pointer value might be different.

Example: When binary value `wr_ptr = 4'b1101` at the write clock domain is transferred via 2FF synchronizer, at the read clock domain `wr_ptr` value may receive as `4'b1111` or any other value that is not acceptable. Whereas gray code is assured to have only a single bit change from its previous value. Hence, both write and read pointers need to convert first to their equivalent gray code in their corresponding domain and then pass them to an opposite domain. To check FIFO full and empty conditions in another domain, we have two ways.

Way 1

Convert received gray code formatted pointers to binary format and then check for the full and empty conditions.

FIFO full condition

```
g2b_converter g2b_wr(Readg_rptr_sync, Readb_rptr_sync); // g2b_converter is a different module
```

```
? wrap_around = b_rptr_sync[PTR_WIDTH] ^ b_wptr[PTR_WIDTH];
```

```
wfull = wrap_around & (b_wptr[PTR_WIDTH-1:0] == b_rptr_sync[PTR_WIDTH-1:0]); // The lower bits (position) of the write and read pointers match.
```

$\text{wrap_around} = \text{MSB of Read ptr sync} \wedge \text{MSB of write ptr}$

$$0 \wedge 1 = 1;$$

FIFO empty condition

```
g2b_converter g2b_rd(Writeg_wptr_sync, Writeb_wptr_sync);
```

```
rempty = (b_wptr_sync == b_rptr_next);
```

Way 2

Check for full and empty conditions directly with the help of gray coded write and read pointer received. This is efficient as it does not need extra hardware for converting gray-coded write and read pointers to equivalent binary forms.

FIFO full condition

```
wfull = (g_wptr_next == {~g_rptr_sync[PTR_WIDTH:PTR_WIDTH-1], g_rptr_sync[PTR_WIDTH-2:0]});
```

FIFO empty condition

```
rempty = (g_wptr_sync == g_rptr_next);
```

Asynchronous FIFO Verilog Code

Write Pointer Handler

The output of synchronizer `g_rptr_sync` is given as an input to 'write pointer handler' module used to generate the FIFO full condition. The binary write pointer (`b_wptr`) is incremented if it satisfies `(w_en & !full)` condition. This `b_wptr` value is fed to the `fifo_mem` module to write data into the FIFO.

```
module wptr_handler #(parameter PTR_WIDTH=3) (  
  input wclk, wrst_n, w_en,  
  input [PTR_WIDTH:0] g_rptr_sync,  
  output reg [PTR_WIDTH:0] b_wptr, g_wptr,  
  output reg full  
);
```

Module Defined

Intermediate
Variables

```
reg [PTR_WIDTH:0] b_wptr_next;  
reg [PTR_WIDTH:0] g_wptr_next; // Next defined
```

```
reg wrap_around;  
wire wfull; // why?
```

If write enable is true and the FIFO is not full, then it increments `b_wptr` by 1.

```
assign b_wptr_next = b_wptr + (w_en & !full);  
assign g_wptr_next = (b_wptr_next >> 1) ^ b_wptr_next; // gray code conversion logic
```

```
always@(posedge wclk or negedge wrst_n) begin  
  if(!wrst_n) begin  
    b_wptr <= 0; // set default value } Reset  
    g_wptr <= 0;  
  end  
  else begin  
    b_wptr <= b_wptr_next; // incr binary write pointer  
    g_wptr <= g_wptr_next; // incr gray write pointer  
  end  
end
```

1st Always
Block

⬆ Binary & Gray
both type of
Pointer.

```
always@(posedge wclk or negedge wrst_n) begin  
  if(!wrst_n) full <= 0; } Reset  
  else full <= wfull; ? } Not  
end
```

wfull → assign wfull = (g_wptr_next == {~g_rptr_sync[PTR_WIDTH:PTR_WIDTH-1],
g_rptr_sync[PTR_WIDTH-2:0]}); // ? imp.
endmodule

The two most significant bits of `g_rptr_sync` (`PTR_WIDTH:PTR_WIDTH-1`) are inverted using ~
The rest of the bits (`PTR_WIDTH-2:0`) remain unchanged.

This creates a "wrap-around condition" for the write pointer to detect when the FIFO is full.

If `g_wptr_next` matches the modified `g_rptr_sync`, it means the FIFO is full.

It takes `b_wptr_next`, shifts it one bit to the right (`b_wptr_next >> 1`),
// gray code conversion logic : and performs a bitwise XOR (^) with the original `b_wptr_next`.

Read Pointer Handler

The output of synchronizer g_wptr_sync is given as an input to the 'read pointer handler' module to generate FIFO empty condition. The binary read pointer (b_rptr) is incremented if it satisfies (r_en & !empty) condition. This b_rptr value is fed to the fifo_mem module to read data from the FIFO.

```
module rptr_handler #(parameter PTR_WIDTH=3) (  
    input rclk, rrst_n, r_en,  
    input [PTR_WIDTH:0] g_wptr_sync,  
    output reg [PTR_WIDTH:0] b_rptr, g_rptr,  
    output reg empty  
);
```

Module Defined

```
    reg [PTR_WIDTH:0] b_rptr_next;  
    reg [PTR_WIDTH:0] g_rptr_next;  
    assign b_rptr_next = b_rptr+(r_en & !empty);  
    assign g_rptr_next = (b_rptr_next >> 1)^b_rptr_next;  
    assign rempty = (g_wptr_sync == g_rptr_next);
```

} // Next defined

```
always@(posedge rclk or negedge rrst_n) begin  
    if(!rrst_n) begin  
        b_rptr <= 0;  
        g_rptr <= 0;  
    end  
    else begin  
        b_rptr <= b_rptr_next;  
        g_rptr <= g_rptr_next;  
    end  
end
```

1st Always Block

```
always@(posedge rclk or negedge rrst_n) begin  
    if(!rrst_n) empty <= 1;  
    else  
        empty <= rempty;  
    end  
endmodule
```

2nd ———

rempty:

This is a combinational signal.

It immediately reflects the result of the comparison (g_wptr_sync == g_rptr_next), indicating whether the FIFO is empty at that exact moment.

It does not depend on the clock and serves as an intermediate condition for the logic.

empty:

This is a registered signal (a flip-flop).

It is updated on the clock edge (posedge rclk), meaning it only changes when the read clock (rclk) pulses.

It reflects the latched state of rempty during the last clock cycle.

Based on binary coded write and read pointers data is written into the FIFO or read from the FIFO respectively.

Module Declarations

```
\include "synchronizer.v"
\include "wptr_handler.v"
\include "rptr_handler.v"
\include "fifo_mem.v"
```

Module Declaration

```

reg [PTR_WIDTH:0] g_wptra_sync, g_rptr_sync; // Synchronized versions of the Gray pointers
reg [PTR_WIDTH:0] b_wptra, b_rptr;           // after crossing domains.
reg [PTR_WIDTH:0] g_wptra, g_rptr; // before crossing domains.

```

```

1a. synchronizer #(PTR_WIDTH) sync_wptr (rclk, rrst_n, g_wptr, g_wptr_sync);
    //write pointer to read clock domain
1b. synchronizer #(PTR_WIDTH) sync_rptr (wclk, wrst_n, g_rptr, g_rptr_sync);
    //read pointer to write clock domain

2a. wptr_handler #(PTR_WIDTH) wptr_h(wclk, wrst_n,
    w_en,g_rptr_sync,b_wptr,g_wptr,full);
2b. rptr_handler #(PTR_WIDTH) rptr_h(rclk, rrst_n,
    r_en,g_wptr_sync,b_rptr,g_rptr,empty);
3. fifo_mem fifom(wclk, w_en, rclk, r_en,b_wptr, b_rptr, data_in,full,empty,
    data_out);

```

endmodule

fifo_mem #(// Optional: Specify parameter values here, if different from default

```

    .DEPTH(8),      // FIFO depth
    .DATA_WIDTH(8), // Data width
    .PTR_WIDTH(3)   // Pointer width

```

Testbench Code

module async_fifo_TB;

parameter DATA_WIDTH = 8;

wire [DATA_WIDTH-1:0] data_out;

wire full;

wire empty;

reg [DATA_WIDTH-1:0] data_in;

reg w_en, wclk, wrst_n;

reg r_en, rclk, rrst_n;

// Queue to push data_in

reg [DATA_WIDTH-1:0] wdata_q[\$], wdata;

asynchronous_fifo as_fifo (wclk, wrst_n,rclk,
rrst_n,w_en,r_en,data_in,data_out,full,empty);

always #10ns wclk = ~wclk;

always #35ns rclk = ~rclk;

initial begin

wclk = 1'b0; wrst_n = 1'b0;

w_en = 1'b0;

data_in = 0;

repeat(10) @(posedge wclk);

wrst_n = 1'b1;

repeat(2) begin

for (int i=0; i<30; i++) begin

@(posedge wclk iff !full);

w_en = (i%2 == 0)? 1'b1 : 1'b0;

if (w_en) begin

data_in = \$urandom;

wdata_q.push_back(data_in);

end

end

#50;

end

```

) fifom (
    .wclk(wclk),      // Connect the wclk signal to the wclk port
    .w_en(w_en),      // Connect the w_en signal to the w_en port
    .rclk(rclk),      // Connect the rclk signal to the rclk port
    .r_en(r_en),      // Connect the r_en signal to the r_en port
    .b_wptr(b_wptr),  // Connect the b_wptr signal to the b_wptr port
    .b_rptr(b_rptr),  // Connect the b_rptr signal to the b_rptr port
    .data_in(data_in), // Connect the data_in signal to the data_in port
    .full(full),      // Connect the full signal to the full port
    .empty(empty),    // Connect the empty signal to the empty port
    .data_out(data_out) // Connect the data_out signal to the data_out port
);

```

```

end

initial begin
    rclk = 1'b0; rrst_n = 1'b0;
    r_en = 1'b0;

    repeat(20) @(posedge rclk);
    rrst_n = 1'b1;

    repeat(2) begin
        for (int i=0; i<30; i++) begin
            @(posedge rclk iff !empty);
            r_en = (i%2 == 0)? 1'b1 : 1'b0;
            if (r_en) begin
                wdata = wdata_q.pop_front();
                if(data_out !== wdata) $error("Time = %0t: Comparison Failed:
expected wr_data = %h, rd_data = %h", $time, wdata, data_out);
                else $display("Time = %0t: Comparison Passed: wr_data = %h and
rd_data = %h", $time, wdata, data_out);
            end
        end
        #50;
    end

    $finish;
end

initial begin
    $dumpfile("dump.vcd"); $dumpvars;
end
endmodule

```

Output:

```
Time = 1575: Comparison Passed: wr_data = 51 and rd_data = 51
Time = 1715: Comparison Passed: wr_data = cd and rd_data = cd
Time = 1855: Comparison Passed: wr_data = 0e and rd_data = 0e
Time = 1995: Comparison Passed: wr_data = db and rd_data = db
Time = 2135: Comparison Passed: wr_data = 71 and rd_data = 71
Time = 2275: Comparison Passed: wr_data = 63 and rd_data = 63
Time = 2415: Comparison Passed: wr_data = e9 and rd_data = e9
Time = 2555: Comparison Passed: wr_data = 98 and rd_data = 98
Time = 2695: Comparison Passed: wr_data = 03 and rd_data = 03
Time = 2835: Comparison Passed: wr_data = a4 and rd_data = a4
Time = 2975: Comparison Passed: wr_data = a7 and rd_data = a7
Time = 3115: Comparison Passed: wr_data = 45 and rd_data = 45
Time = 3255: Comparison Passed: wr_data = 00 and rd_data = 00
Time = 3395: Comparison Passed: wr_data = 4f and rd_data = 4f
Time = 3535: Comparison Passed: wr_data = 3e and rd_data = 3e
Time = 3675: Comparison Passed: wr_data = e7 and rd_data = e7
Time = 3815: Comparison Passed: wr_data = d8 and rd_data = d8
Time = 3955: Comparison Passed: wr_data = 31 and rd_data = 31
Time = 4095: Comparison Passed: wr_data = 8b and rd_data = 8b
Time = 4235: Comparison Passed: wr_data = 07 and rd_data = 07
Time = 4375: Comparison Passed: wr_data = a1 and rd_data = a1
Time = 4515: Comparison Passed: wr_data = 15 and rd_data = 15
Time = 4655: Comparison Passed: wr_data = e6 and rd_data = e6
Time = 4795: Comparison Passed: wr_data = 80 and rd_data = 80
Time = 4935: Comparison Passed: wr_data = 01 and rd_data = 01
Time = 5075: Comparison Passed: wr_data = 72 and rd_data = 72
Time = 5215: Comparison Passed: wr_data = c8 and rd_data = c8
Time = 5355: Comparison Passed: wr_data = dc and rd_data = dc
Time = 5495: Comparison Passed: wr_data = d7 and rd_data = d7
```